NYCU EE-VLSI 2022

Final Project: 6-Bit Multiplier and Accumulator Design

Due at 2022/01/09 12:00

I. Abstract

In this lab, you are required to design a 6-bit MAC with Two-Mode in full custom design. This document includes the specification and requirement of your design, and grading policy.

 


Fig 2. Pipeline example

II. Please design a 6-bit multiplier and accumulator. The design specifications are given as follows:

• File name: MAC6.sp

Sub-circuit name: MAC6 (including top cell name in layout)
Input port (signed): A [5:0], B [5:0], ACC [11:0], MODE, CLK

• Output port(signed): OUT [12:0]

III. The specification is described as the following:

✓ Rise time and fall time of input signal: 0.1ns

✓ Output loading of OUT [12:0]: 10f

- ✓ Supply voltage: 1.8V
- ✓ Only metal 1 ~ metal 6 are allowed, others are prohibited.
- **IV.** Try to optimize your design as possible as you can. A suggested performance of your design (under TT case):
 - ✓ Maximum propagation delay should be shorter as possible as you can.
 - ✓ Peak power & average power should be improved as possible as you can.
 - ✓ The art of layout will be considered and discussed for this work.
 - ✓ Try to reduce parasitic capacitance and resistance to narrow the gap between pre-sim and post-sim performance.
 - \checkmark Area is defined as the smallest rectangle which includes whole layout, and the rectangle ratio should fall in the range of 2 ~ 0.5 as possible.

V. Grading Policy:

- 1. Pre-sim (HSPICE): 15%
- 2. Layout: 20% (partial scoring)
- 3. DRC, LVS: 10%
- 4. Post-sim (HSPICE): 10%
- 5. Performance: 25%
 - (1) Pre-sim frequency: 5% (need to pass pre-sim with SPEC in III.)
 - (2) Layout Figure-of-merit(FoM) = (Layout area)*(Post-sim Period)*(Power) 20%

Note that: Layout area including N-well, need to pass DRC and LVS verification and need to pass post-sim with SPEC in III.

- 6. Report: 20%
 - (1) Please follow attached report format for this part.

Note:

1. Copy the files to your own account:

"tar -xvf ~vlsita01/Final_Proj_2022.tar"

- 2. RTL part is provided for you to design the circuit from system level. Use it or not depends on you and won't be graded.
- 3. You need to hand in the following files on New E3

File	Description				
(1) studentID_MAC6.gds	From LVS directory				
(2) studentID_MAC6.sp	Pre-sim design. Only add codes under the line 61				
	(comment) and submit this part; do not touch the part				
	above except for cycle period.				
(3) studentID_period.txt	List your pre-sim clock period and post-sim clock period.				
	Pre-sim: ### ns				
	Post-sim: ### ns				
Syct	(you must follow the attached format)				
(4) studentID_report.pdf	Just report				

- 4. Since a script for standard verification flow is used for demo in this project, make sure that submitted pre-sim file is consistent with layout file, e.g. port names, MOS width and so on.
- 5. Naming error rules: (You will get 5-point penalty if you break any of the followingrules)
 - (1) File names are consistent with the table above. DON'T submit compressed files.
 - (2) For studentID_MAC6.sp, only codes under the line 61 (comment) are submit.
 - (3) Please use P_18_G2 and N_18_G2 as MOS model in studentID_MAC6.sp
 - (4) Do NOT modify port names, VDD, GND and CLK in your pre-sim file and layout.
 - (5) Student ID, which is first one of your team members, need to be same in the four file names.

Team No.	Team Name	Member #1	Member #2	Member #3
0	統神端火鍋	▲ 甄基極	艾閘極	倪涉極

- 6. You can make good use of forum on Facebook in there is any ambiguity in this project and document.
- 7. Enjoy the fun from this assigned work